

Chapter Four:

Register Transfer and Microoperations

Contents to be covered

- **Register Transfer Language**
- **Register Transfer**
- **Bus and Memory Transfers**
- **Arithmetic Microoperations**
- **Logic Microoperations**
- **Shift Microoperations**

4-1 Register Transfer Language (RTL)

- Simple digital Systems are an interconnection of hardware modules that do a certain task on the information.
- The modules are constructed from such digital components as registers, decoders, arithmetic elements and control logic
- Modules are interconnected with common data and control paths to form a digital computer system
- The internal organization of a digital system is defined by the sequence of micro operations it performs on data stored in its registers.
- The general-purpose digital computer is **capable of executing various micro operations** and, in addition, can be instructed as to **what specific sequence of operations** it must perform.

4-1 Register Transfer Language (RTL)

- The user of a computer can control the process by means of a program.
- A program is a set of instructions that specify the operations, operations operands, and the sequence by which processing has to occur.
- A computer instruction is a binary code that specifies a sequence of micro operations for the computer.
- **What is microoperation?**

4-1 Register Transfer Language ^{cont.}

- **Microoperations**: are operations executed on data stored in one or more registers.
- The result of the operation may be:
 - replace the previous binary information of a register or
 - transferred to another register



- The microoperations most often encountered in *digital computers* are classified into four categories:
 - **Register transfer micro-operations**
 - **Arithmetic micro-operations**
 - **Logic micro-operations**
 - **Shift micro-operations**

4-1 Register Transfer Language ^{cont.}


- The internal hardware organization of a digital computer is defined by specifying:
 - The set of registers it contains and their function
 - The sequence of microoperations performed on the binary information stored in the registers
 - The control that initiates the sequence of microoperations
- **Register Transfer Language (RTL)** : a symbolic notation to describe the microoperation transfers among registers

4-2 Register Transfer (our first microoperation)


- Computer registers are designated by capital letters (sometimes followed by numerals) to denote the function of the register
 - R1: processor register
 - MAR: Memory Address Register (holds an address for a memory unit)
 - PC: Program Counter
 - IR: Instruction Register
 - SR: Status Register

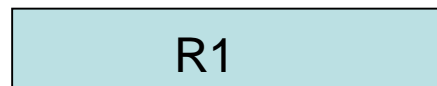4-2 Register Transfer ^{cont.}

- The individual flip-flops in an n-bit register are numbered in sequence from 0 to n-1 (from the right position toward the left position)



Register R1

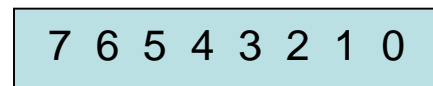


Showing individual bits


A block diagram of a register

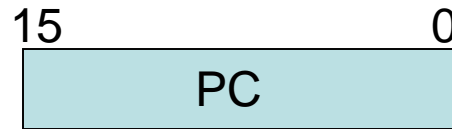4-2 Register Transfer ^{cont.}

Other ways of drawing the block diagram of a register:



Numbering of bits

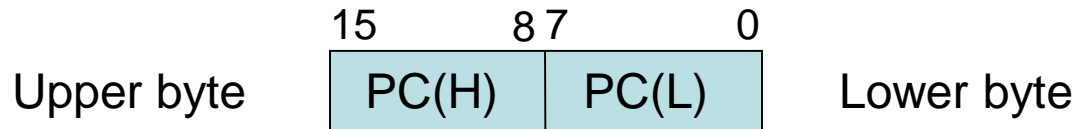

Partitioned into two parts

4-2 Register Transfer ^{cont.}

- Information transfer from one register to another is described by a *replacement operator*: $\mathbf{R2} \leftarrow \mathbf{R1}$
 - This statement denotes a transfer of the content of register R1 into register R2
 - The transfer happens in one clock cycle
 - The content of the R1 (source) does not change
 - The content of the R2 (destination) will be lost and replaced by the new data transferred from R1
- We are assuming that the circuits are available from the outputs of the source register to the inputs of the destination register, and that the destination register has a parallel load capability

4-2 Register Transfer ^{cont.}

- Conditional transfer occurs only under a control condition

If($p=1$) then ($R2 \leftarrow R1$)

- Representation of a (conditional) transfer

P: $R2 \leftarrow R1$

- A binary condition (P equals to 0 or 1) determines when the transfer occurs
- The content of R1 is transferred into R2 only if P is 1


4-2 Register Transfer ^{cont.}

Basic Symbols for Register Transfers


Symbol	Description	Examples
Letters & numerals	Denotes a register	MAR, R2
Parenthesis ()	Denotes a part of a register	R2(0-7), R2(L)
Arrow \leftarrow	Denotes transfer of information	R2 \leftarrow R1
Comma ,	Separates two microoperations	R2 \leftarrow R1, R1 \leftarrow R2

Connecting registers with multiplexers

- Paths must be provided to transfer information from one register to another
- To connect *n items* with direct connections, you need $n(n-1)/2$ connections.
- To connect *n items* with bus connections, you need only n connections.
- A **Common Bus System** is a scheme for transferring information between registers in a **multiple-register configuration**
- A **bus**: set of common lines, one for each bit of a register, through which binary information is transferred one at a time

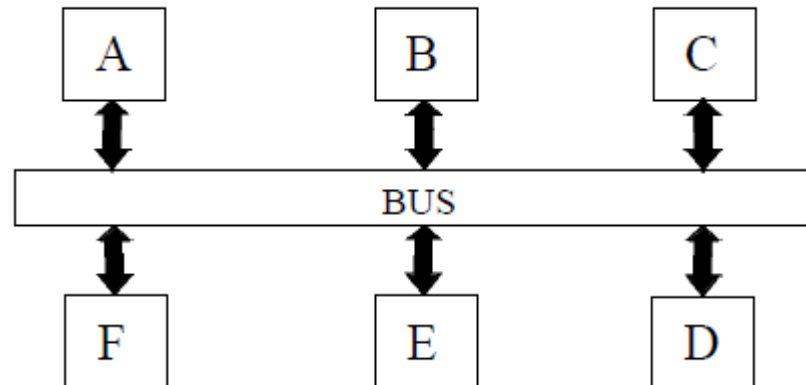

Connecting registers with multiplexers

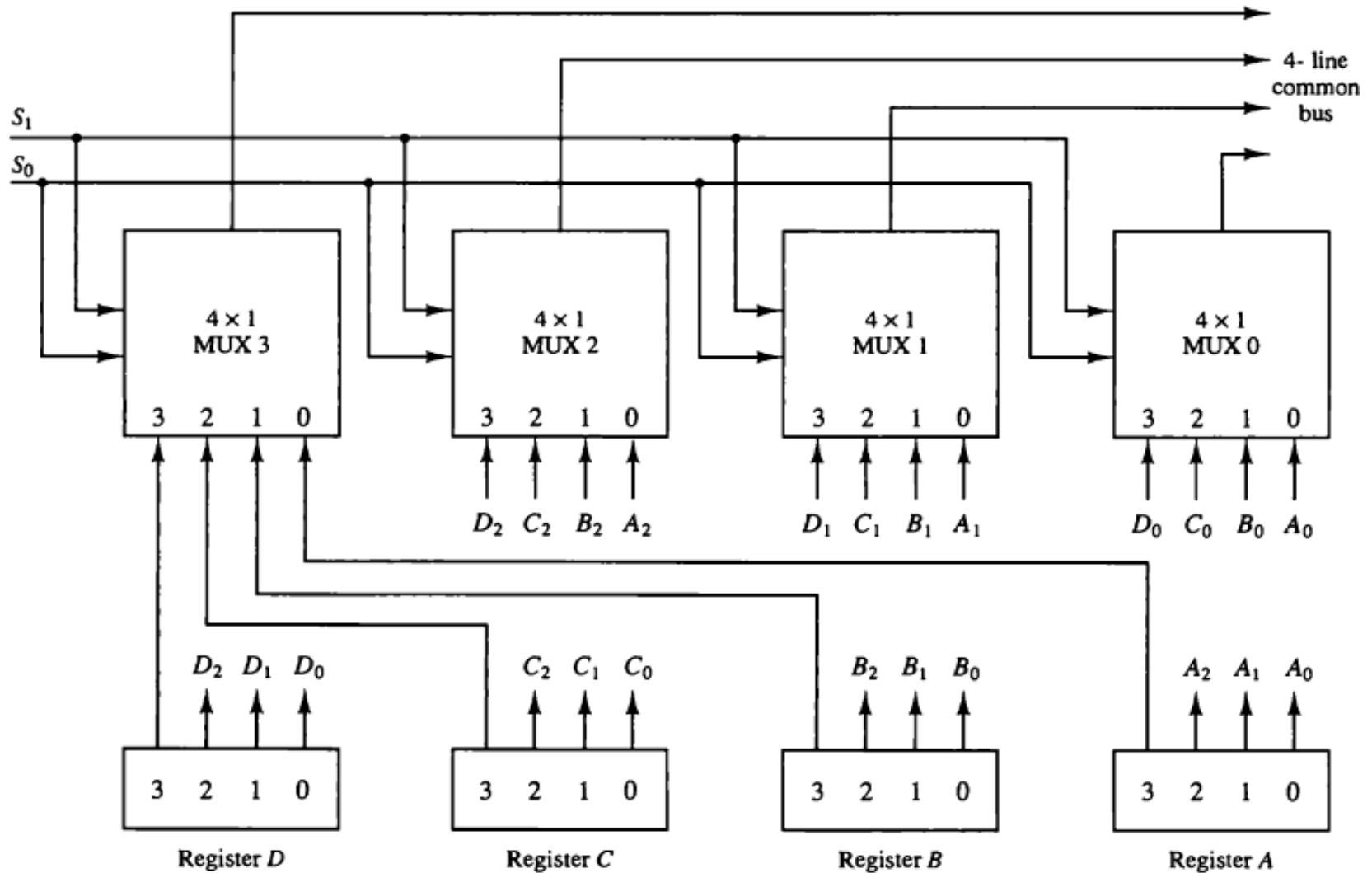

Connecting registers with multiplexers

- The multiplexer selects one of the four registers as the source register.
- **Control signals** determine which register is selected by the bus during each particular register transfer
- External hardware generates **load signals** for the four registers such that no more than one is active at any given time.
- The selection lines choose the four bits of one register and transfer them in to the four line common bus.

Control lines for the mux are driven by external circuitry.

S_1	S_0	Register selected
0	0	<i>A</i>
0	1	<i>B</i>
1	0	<i>C</i>
1	1	<i>D</i>


Connecting registers with multiplexers

- In general, a bus system will multiplex k registers of n bits each to produce an n line common bus
 - This requires n multiplexers – one for each bit
 - The size of each multiplexer must be $k \times 1$
- The transfer of information from a bus into one of many destination registers is done:
 - By connecting the bus lines to the inputs of all destination registers and then:
 - activating the **load control** of the particular destination register selected
- We write: $R2 \leftarrow C$ to symbolize that the content of register C is loaded into the register R2 using the common system bus
- It is equivalent to: $BUS \leftarrow C, (\text{select } C)$


$R2 \leftarrow BUS (\text{Load } R2)$

Connecting registers with Three-State Bus Buffers

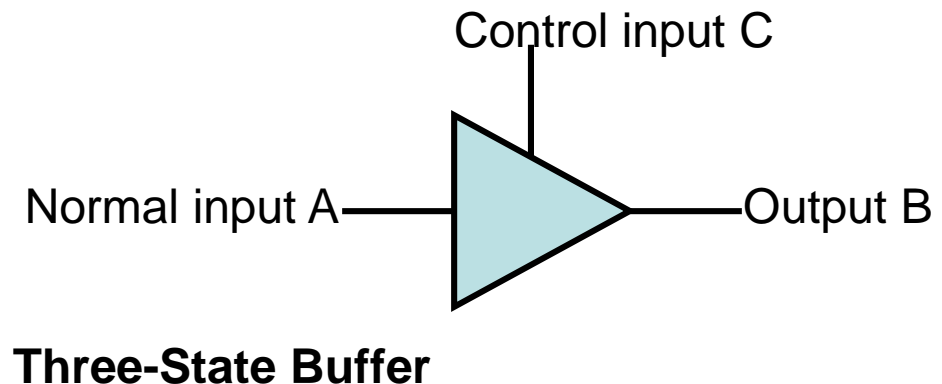
- A bus system can be constructed with **three-state buffer gates** instead of multiplexers
- A three-state buffer is a digital circuit that exhibits three states: logic-0, logic-1, and high-impedance.
- The high impedance state behaves like an open circuit, which means that the output is disconnected and does not have a logic significance.



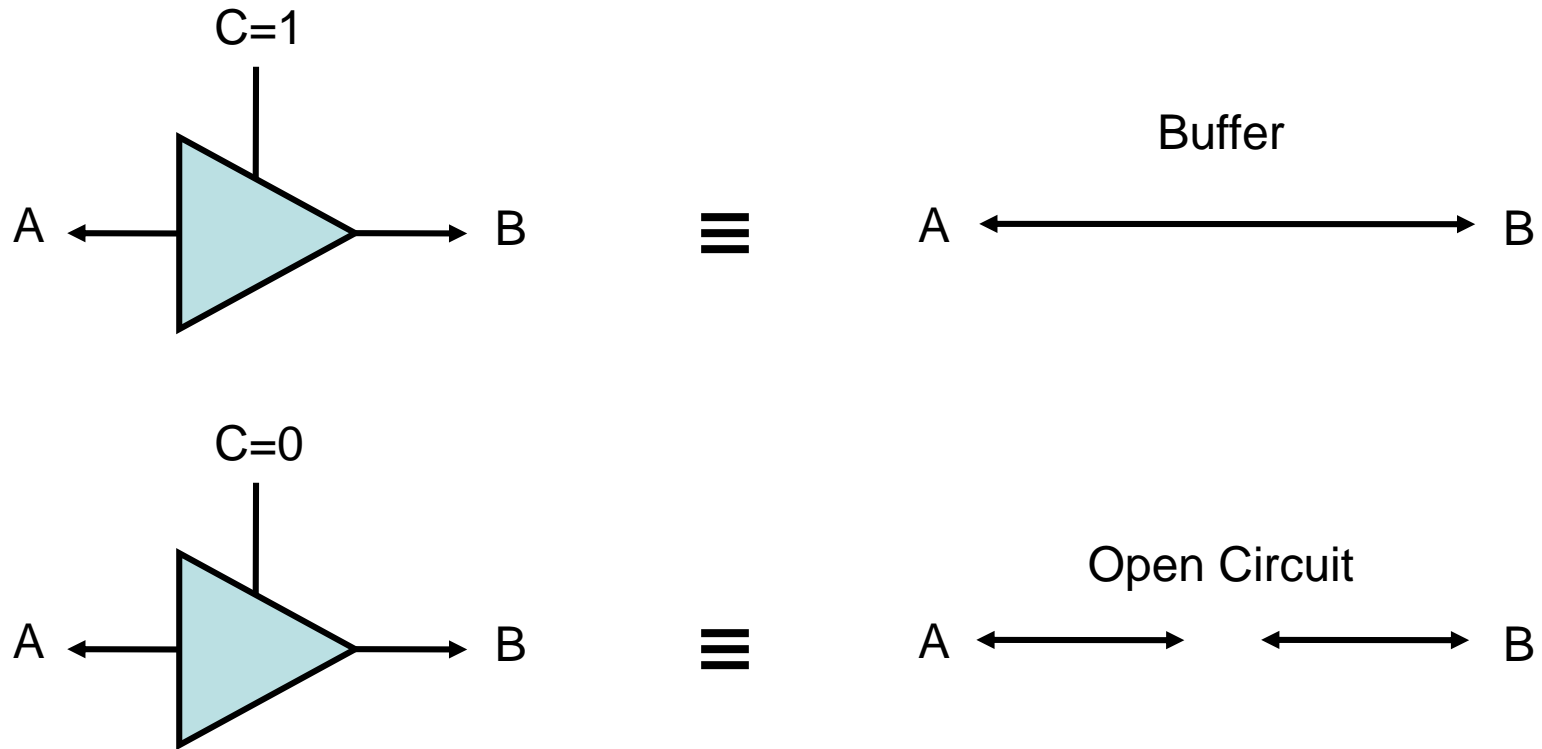Connecting registers with Three-State Bus Buffers



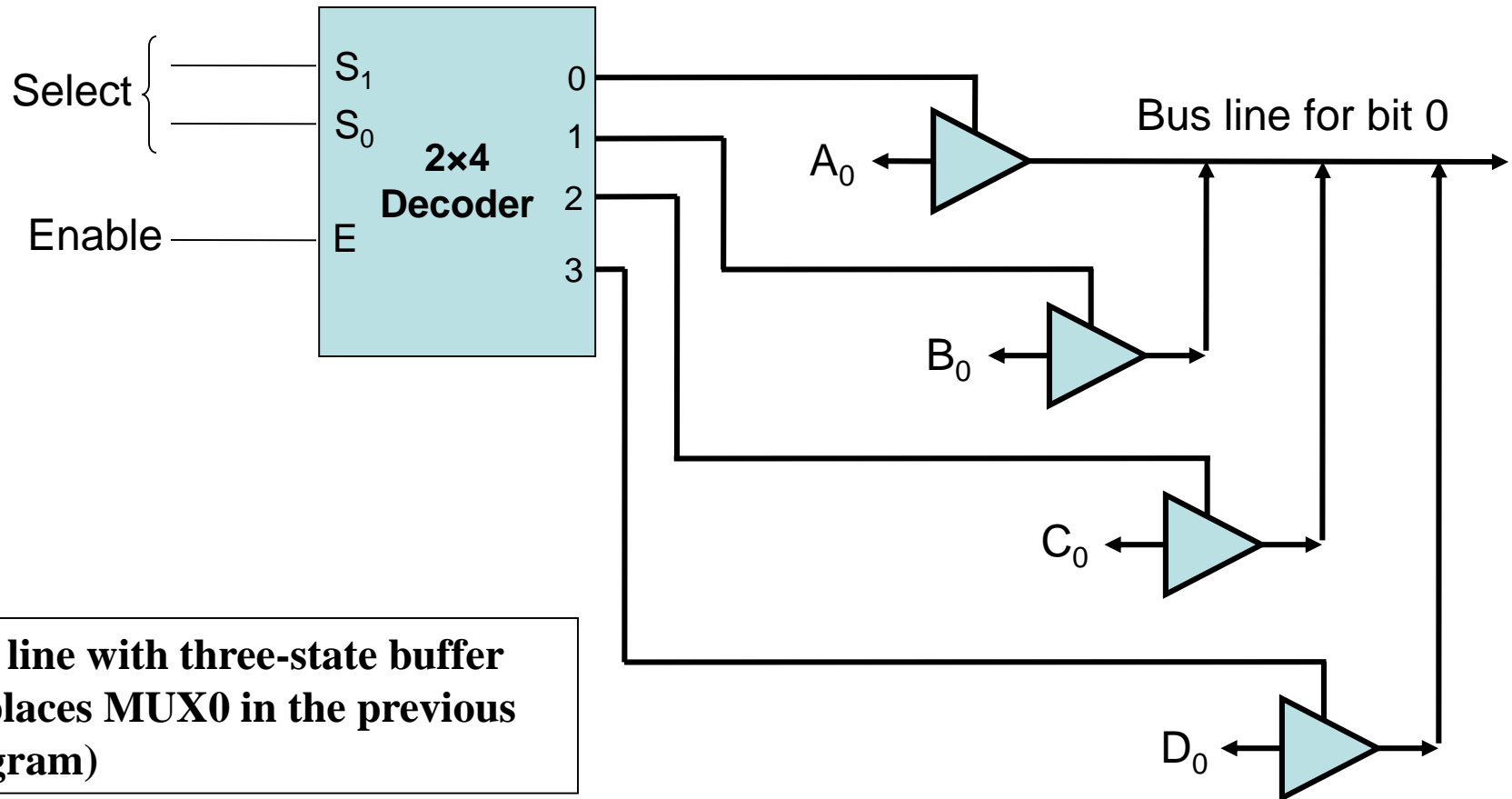Connecting registers with Three-State Bus Buffers




4-3 Bus and Memory Transfers:

- A **memory unit** is a collection of storage cells together with associated circuits needed to transfer information in and out of storage.
- The memory stores binary information in groups of bits called *words*
 - Data being read or wrote is called a memory word (M)
- It is necessary to specify the address of M when writing /reading memory
- This is done by enclosing the address in square brackets following the letter M
 - Example: M[0016] : the memory contents at address 0016

4-3 Bus and Memory Transfers:

- The transfer of information from a memory word to the outside environment is called a **read operation**.
 - **Memory read** : Transfer from memory
- The transfer of new information to be stored into the memory is called a **write operation**.
 - **Memory write** : Transfer to memory
- Assume that the address of a memory unit is stored in a register called the Address Register AR
- Lets represent a Data Register with DR, then:
 - Read: $DR \leftarrow M[AR]$
 - Write: $M[AR] \leftarrow DR$

4-3 Bus and Memory Transfers:

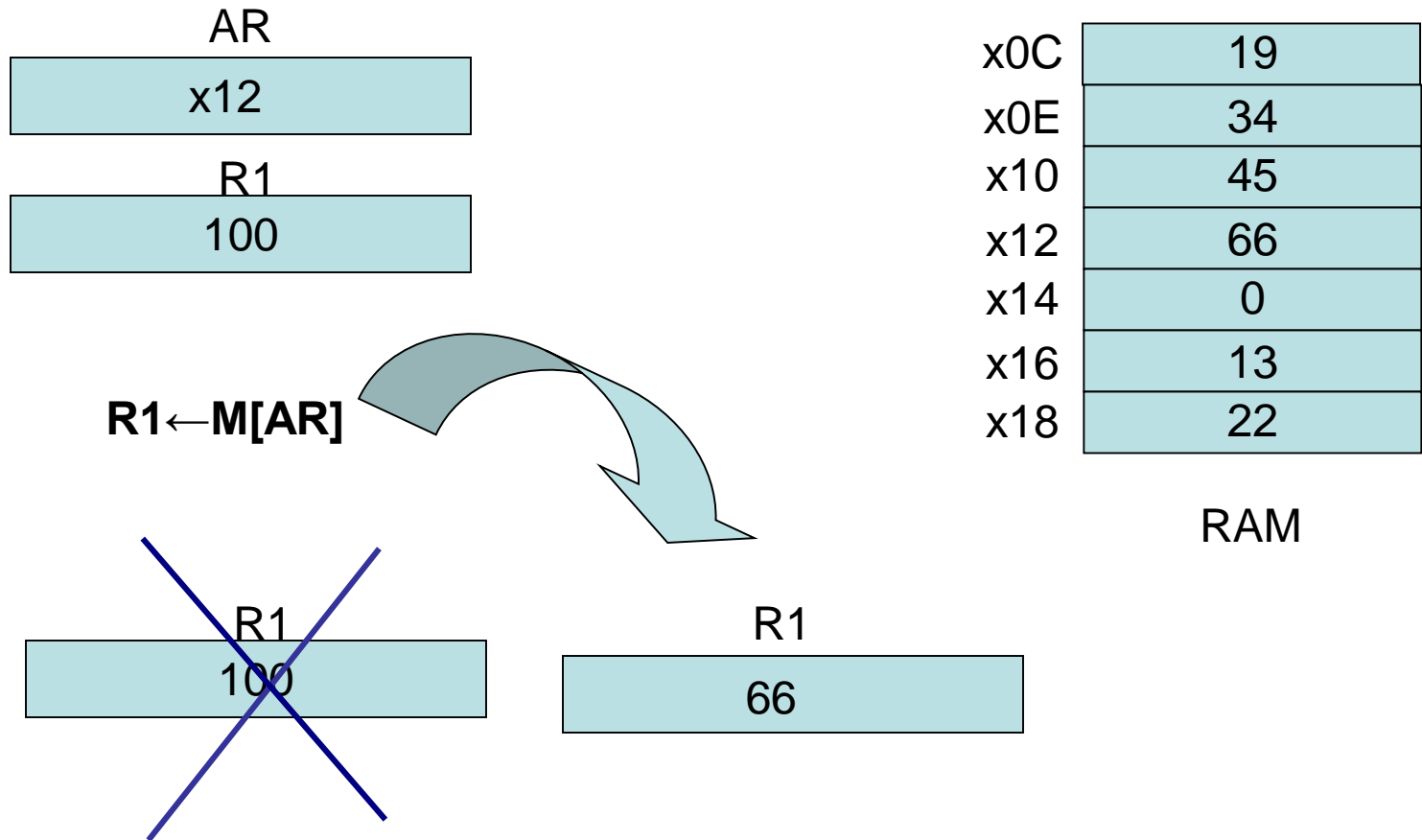


4-4 Arithmetic Microoperations ^{cont.}

- The basic arithmetic microoperations are: addition, subtraction, increment, decrement, and shift
- The following table shows the arithmetic microoperation


Symbolic designation	Description
$R3 \leftarrow R1 + R2$	Contents of $R1$ plus $R2$ transferred to $R3$
$R3 \leftarrow R1 - R2$	Contents of $R1$ minus $R2$ transferred to $R3$
$R2 \leftarrow \overline{R2}$	Complement the contents of $R2$ (1's complement)
$R2 \leftarrow \overline{R2} + 1$	2's complement the contents of $R2$ (negate)
$R3 \leftarrow R1 + \overline{R2} + 1$	$R1$ plus the 2's complement of $R2$ (subtraction)
$R1 \leftarrow R1 + 1$	Increment the contents of $R1$ by one
$R1 \leftarrow R1 - 1$	Decrement the contents of $R1$ by one

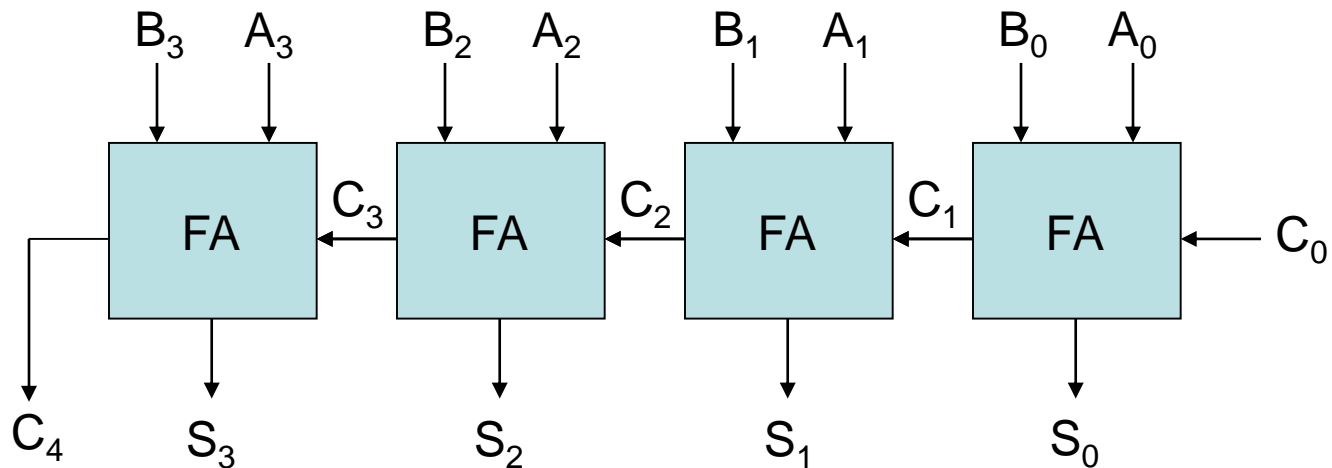4-4 Arithmetic Microoperations: **Binary Adder**



**4-bit binary adder
(connection of FAs)**

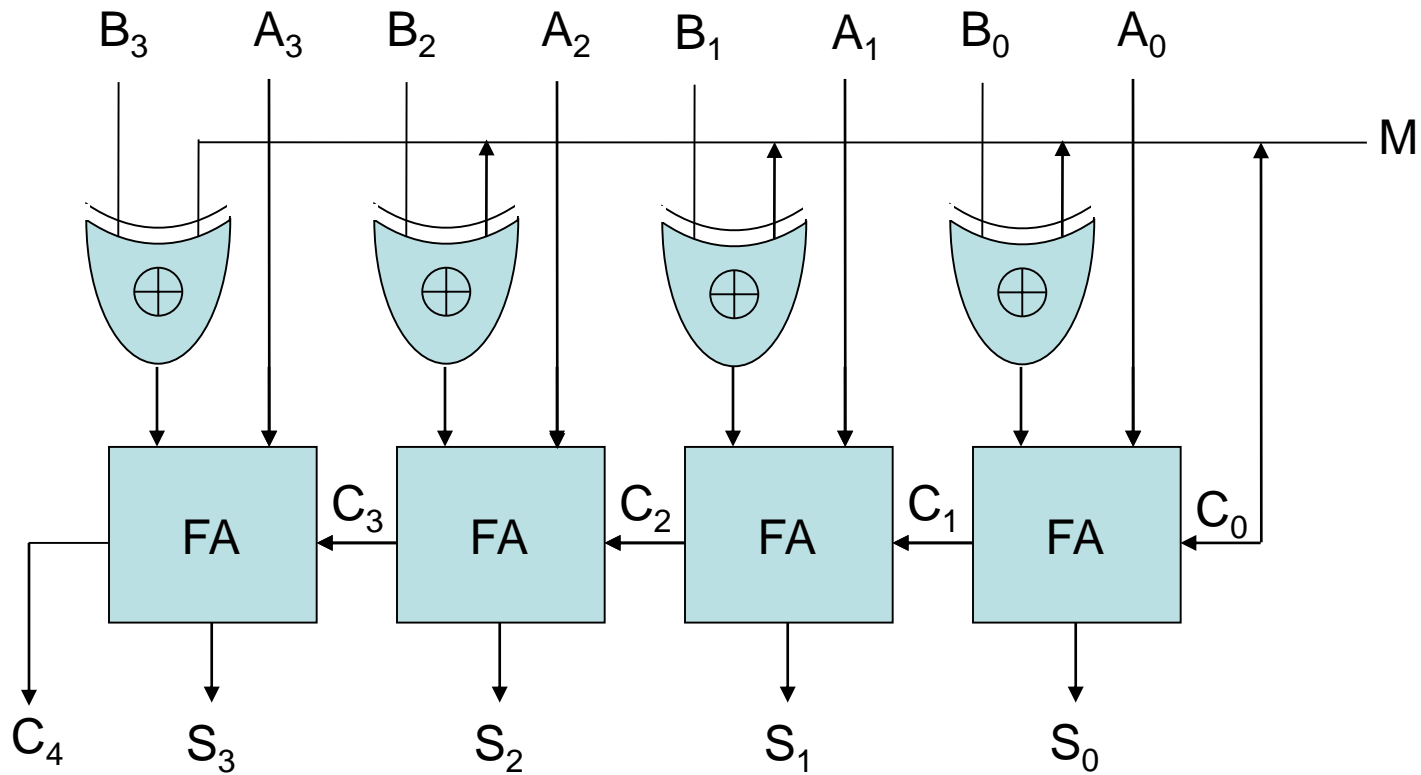4-4 Arithmetic Microoperations: **Binary Adder-Subtractor**



4-bit adder-subtractor

4-4 Arithmetic Microoperations: Binary Adder-Subtractor

- The mode input M controls the operation
- When M=0, the circuit is an adder and
 $B \oplus 0 = B$ and the input carry is 0, then $A+B$
- When M=1, the circuit becomes subtractor

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0


$B \oplus 1 = B'$ and the input carry is 1, then A plus 2's complement of B

The subtraction $A-B$ can be carried out by the following steps

- Take the 1's complement of B
- Get the 2's complement by adding 1
- Add the result to A

4-4 Arithmetic Microoperations: **Binary Incrementer**

4-bit binary incrementer:

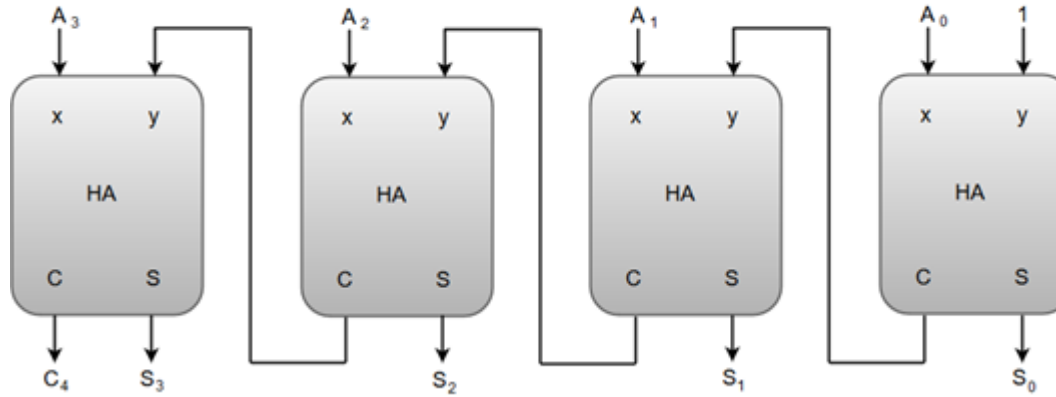

Binary Incrementer

- Binary Incrementer can also be implemented using a counter
- A binary decrementer can be implemented by adding 1111 to the desired register each time!

- **4-5 Logic Microoperations**

- Manipulating the **bits** stored in a register (bit by bit)
- The four basic logic microoperations

Symbolic designation	Description
$R0 \leftarrow \overline{R1}$	Logical bitwise NOT
$R0 \leftarrow R1 \wedge R2$	Logical bitwise AND
$R0 \leftarrow R1 \vee R2$	Logical bitwise OR ()
$R0 \leftarrow R1 \oplus R2$	Logical bitwise XOR


4-5 Logic Microoperations

The four basic microoperations


OR Microoperation

- Symbol: \vee , +

- Gate:

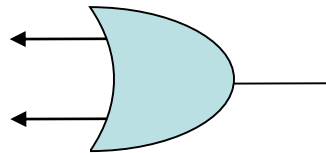

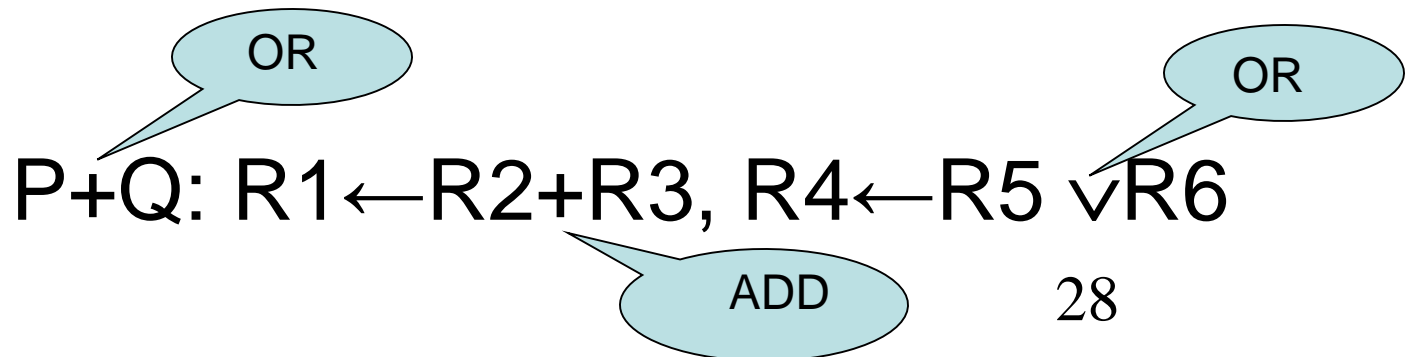- Example: $100110_2 \vee 1010110_2 = 1110110_2$



4-5 Logic Microoperations

The four basic microoperations ^{cont.}

AND Microoperation

- Symbol: \wedge

- Gate: 


- Example: $100110_2 \wedge 1010110_2 = 0000110_2$

4-5 Logic Microoperations

The four basic microoperations ^{cont.}

Complement (NOT) Microoperation

- Symbol: $\overline{}$

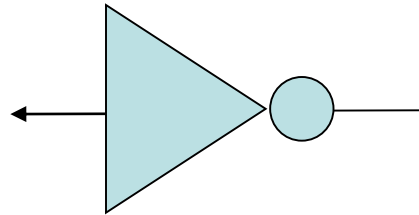

- Gate:

- Example: $\overline{1010110_2} = 0101001_2$


4-5 Logic Microoperations

The four basic microoperations ^{cont.}

XOR (Exclusive-OR) Microoperation

- Symbol: \oplus

- Gate:

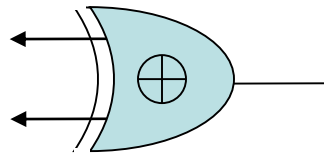

- Example: $100110_2 \oplus 1010110_2 = 1110000_2$

4-5 Logic Microoperations

Other Logic Microoperations

Selective-set Operation


- Used to force selected bits of a register into logic-1 by using the OR operation

- Example: $0100_2 \vee 1000_2 = 1100_2$

In a processor register



Loaded into a register from
memory to perform the
selective-set operation



4-5 Logic Microoperations

Other Logic Microoperations ^{cont.}

Selective-complement (toggling) Operation

- Used to force selected bits of a register to be complemented by using the XOR operation

- Example: $0001_2 \oplus 1000_2 = 1001_2$

In a processor register

Loaded into a register from
memory to perform the
selective-complement operation


4-5 Logic Microoperations

Hardware Implementation

- The hardware implementation of logic microoperations requires that logic gates be inserted for each bit or pair of bits in the registers to perform the required logic function
- Most computers use only four (AND, OR, XOR, and NOT) from which all others can be derived.

4-5 Logic Microoperations

Hardware Implementation ^{cont.}

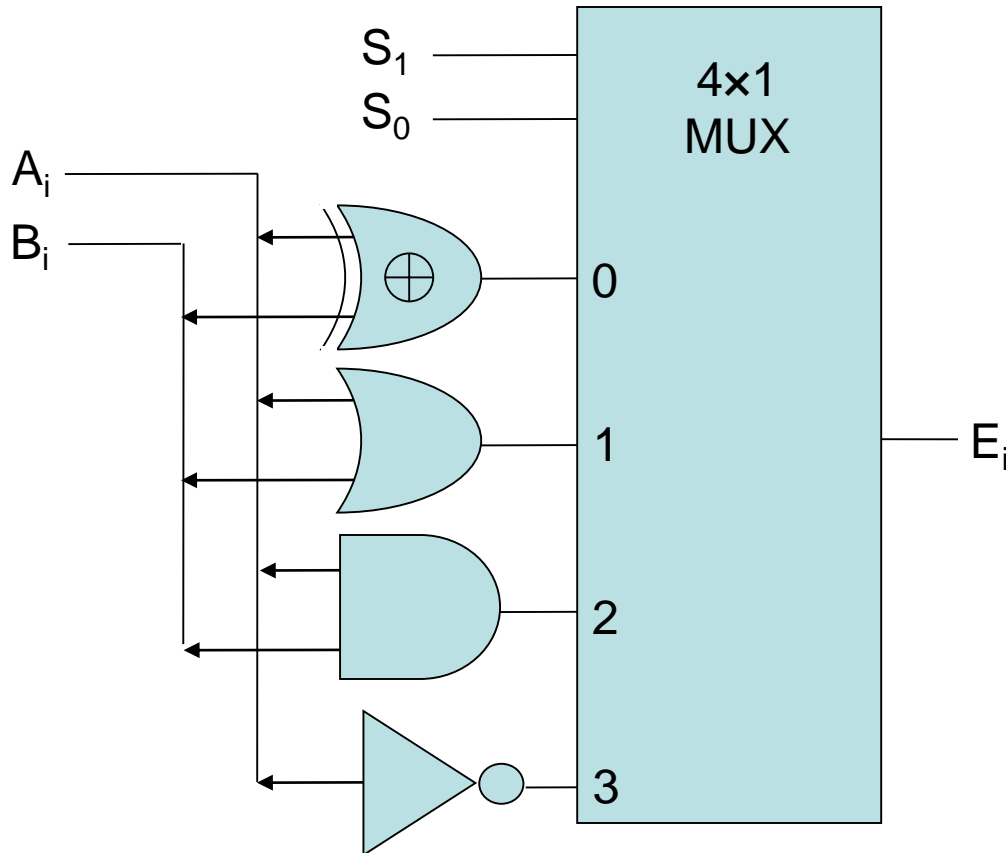

S_1	S_0	Output	Operation
0	0	$E = A \oplus B$	XOR
0	1	$E = A \vee B$	OR
1	0	$E = A \wedge B$	AND
1	1	$E = \overline{A}$	Complement

This is for one bit i

4-5 Logic Microoperations

- List of logic microoperations

Boolean function	Microoperation	Name
$F_0 = 0$	$F \leftarrow 0$	Clear
$F_1 = xy$	$F \leftarrow A \wedge B$	AND
$F_2 = xy'$	$F \leftarrow A \wedge \overline{B}$	
$F_3 = x$	$F \leftarrow A$	Transfer A
$F_4 = x'y$	$F \leftarrow \overline{A} \wedge B$	
$F_5 = y$	$F \leftarrow B$	Transfer B
$F_6 = x \oplus y$	$F \leftarrow A \oplus B$	Exclusive-OR
$F_7 = x + y$	$F \leftarrow A \vee B$	OR
$F_8 = (x + y)'$	$F \leftarrow \overline{A \vee B}$	NOR
$F_9 = (x \oplus y)'$	$F \leftarrow \overline{A \oplus B}$	Exclusive-NOR
$F_{10} = y'$	$F \leftarrow \overline{B}$	Complement B
$F_{11} = x + y'$	$F \leftarrow A \vee \overline{B}$	
$F_{12} = x'$	$F \leftarrow \overline{A}$	Complement A
$F_{13} = x' + y$	$F \leftarrow \overline{A} \vee B$	
$F_{14} = (xy)'$	$F \leftarrow \overline{A \wedge B}$	NAND
$F_{15} = 1$	$F \leftarrow \text{all 1's}$	Set to all 1's

4-6 Shift Microoperations


- Used for serial transfer of data
- Also used in conjunction with arithmetic, logic, and other data-processing operations
- The contents of the register can be shifted to the left or to the right
- As being shifted, the first flip-flop receives its binary information from the serial input
- There are three types of shifts:
 - **Logical shift,**
 - **Circular shift (rotate operation)**
 - **Arithmetic shift**

4-6 Shift Microoperations

- The following table shows shift microoperations

Symbolic designation	Description
$R \leftarrow \text{shl } R$	Shift-left register R
$R \leftarrow \text{shr } R$	Shift-right register R
$R \leftarrow \text{cil } R$	Circular shift-left register R
$R \leftarrow \text{cir } R$	Circular shift-right register R
$R \leftarrow \text{ashl } R$	Arithmetic shift-left R
$R \leftarrow \text{ashr } R$	Arithmetic shift-right R


4-6 Shift Microoperations ^{cont.}

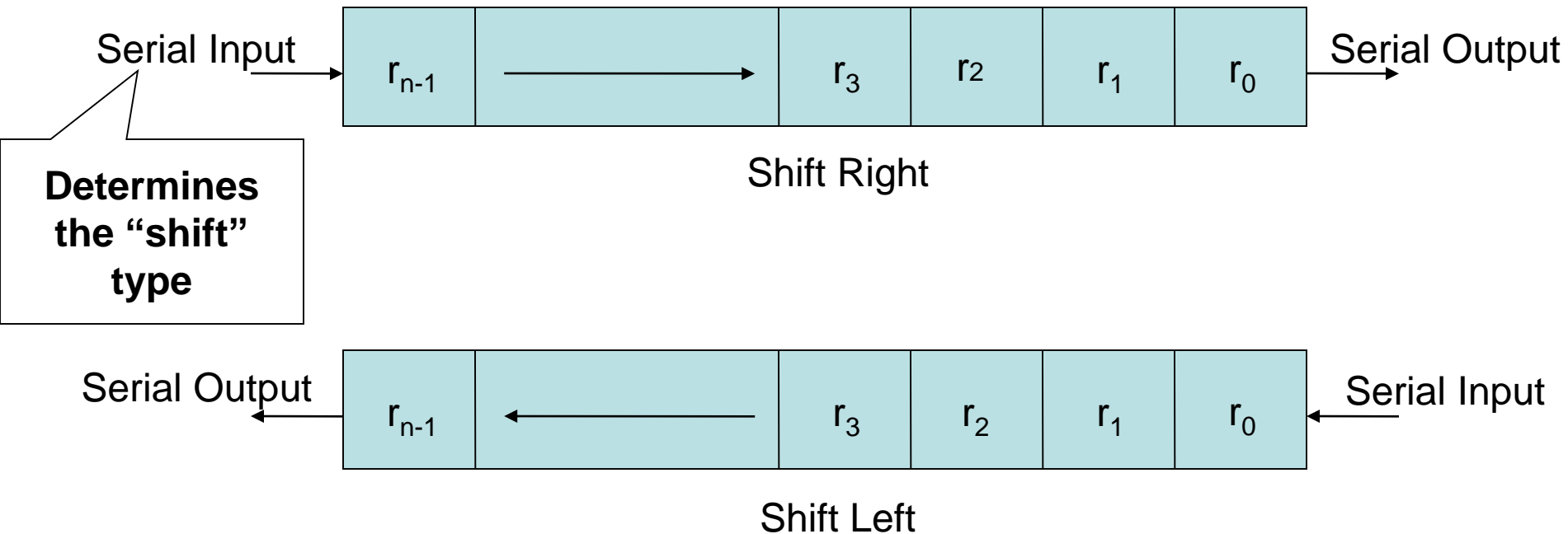


******Note that the bit r_i is the bit at position (i) of the register

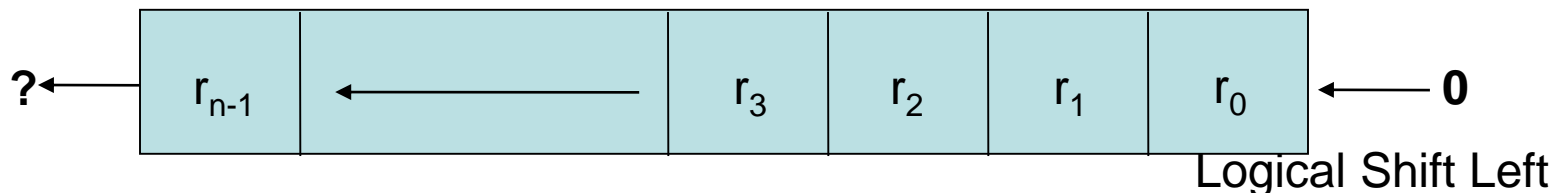4-6 Shift Microoperations: Logical Shifts

- A logical Shift transfers 0 through the serial input (**Zero inserted**)
- Logical Shift Right: $R1 \leftarrow \text{shr } R1$ The same
- Logical Shift Left: $R2 \leftarrow \text{shl } R2$ The same




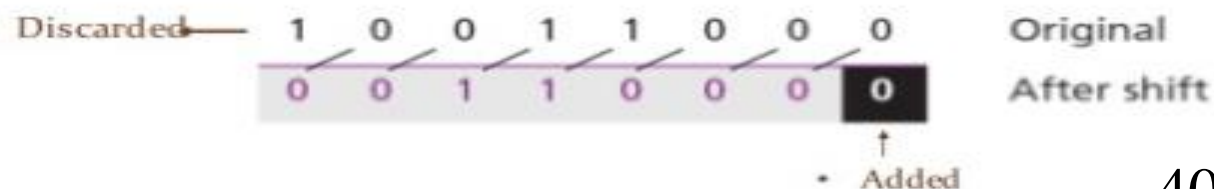- Example: use a logical shift left on the bit pattern 10011000.
- Solution: The leftmost bit is lost and a **0 is inserted as the rightmost bit.**




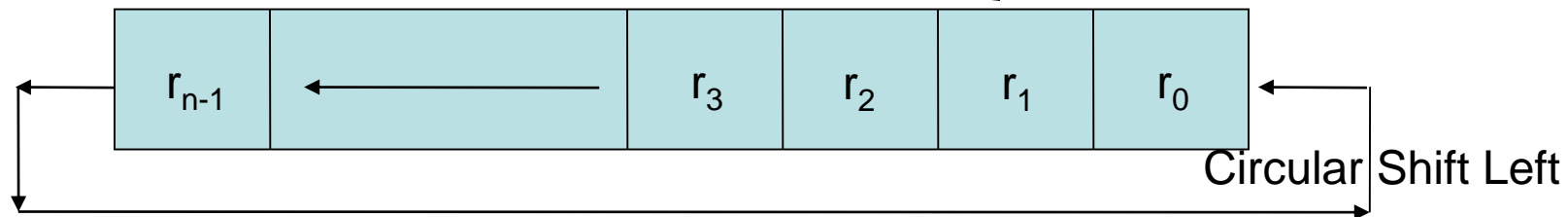4-6 Shift Microoperations: Circular Shifts (Rotate Operation)

- Circulates the bits of the register around the two ends **without loss of information**
- Circular Shift Right: $R1 \leftarrow \text{cir } R1$
- Circular Shift Left: $R2 \leftarrow \text{cil } R2$



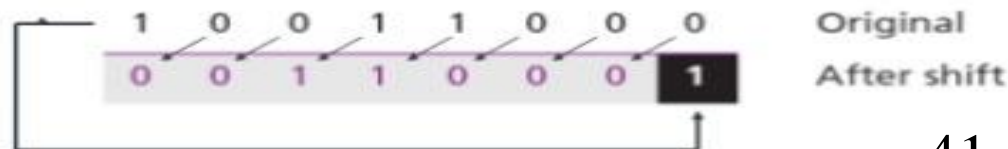- Use a Circular Left Shift Operation on the bit pattern **10011000**.
- Solution: The leftmost bit is circulated and becomes the rightmost bit.



4-6 Shift Microoperations

Arithmetic Shifts

- Shifts a **signed binary number** to the left or right
- An arithmetic **shift-left multiplies** a signed binary number by 2: `ashl (00100): 01000`
- An arithmetic **shift-right divides** the number by 2
`ashr (00100) : 00010`
- The sign bit is 0 for positive and 1 for negative.




4-6 Shift Microoperations

Arithmetic Shifts ^{cont.}

- An overflow may occur in arithmetic shift-left, and occurs when the **sign bit is changed** (sign reversal)
- An overflow flip-flop V_s can be used to detect an arithmetic shift-left overflow


$$V_s = R_{n-1} \oplus R_{n-2}$$

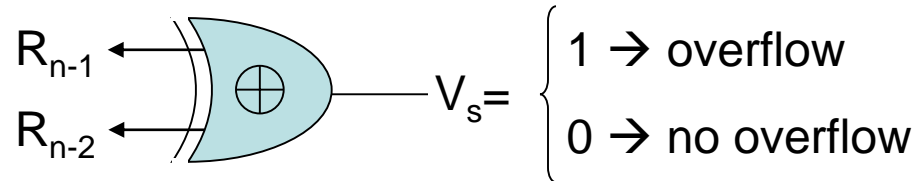

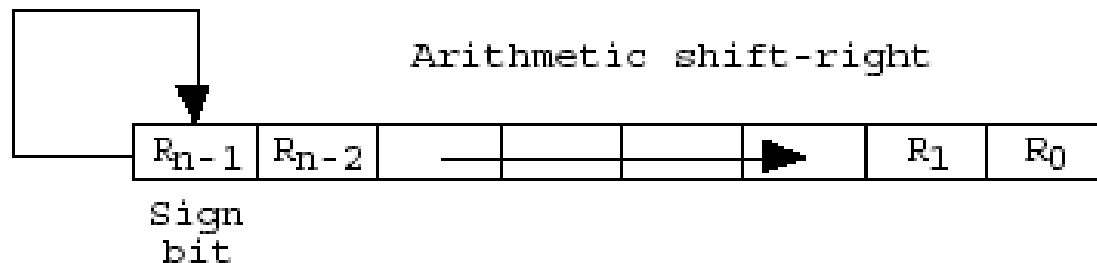4-6 Shift Microoperations

Arithmetic Shifts

- **Arithmetic shift right:**
 - R_{n-1} remains unchanged;
 - R_{n-2} receives R_{n-1} , R_{n-3} receives R_{n-2} , so on.
- For a negative number, 1 is shifted from the sign bit to the right.
- A negative number is represented by the **2's complement** form. The sign bit remained unchanged.



4-6 Shift Microoperations

Arithmetic Shifts

- **Arithmetic Shift Right :**

- Example 1

0100 (4) \rightarrow 0010 (2)

- Example 2

1010 (-6) \rightarrow 1101 (-3)

4-6 Shift Microoperations


Arithmetic Shifts

Arithmetic Shift Left

- The operation is same with **Logic shift-left**
 - transfers 0 through the serial input (**Zero inserted**)
- **The only difference is you need to check overflow problem**

Carry out
Sign bit

$R2 \leftarrow ashl R2$

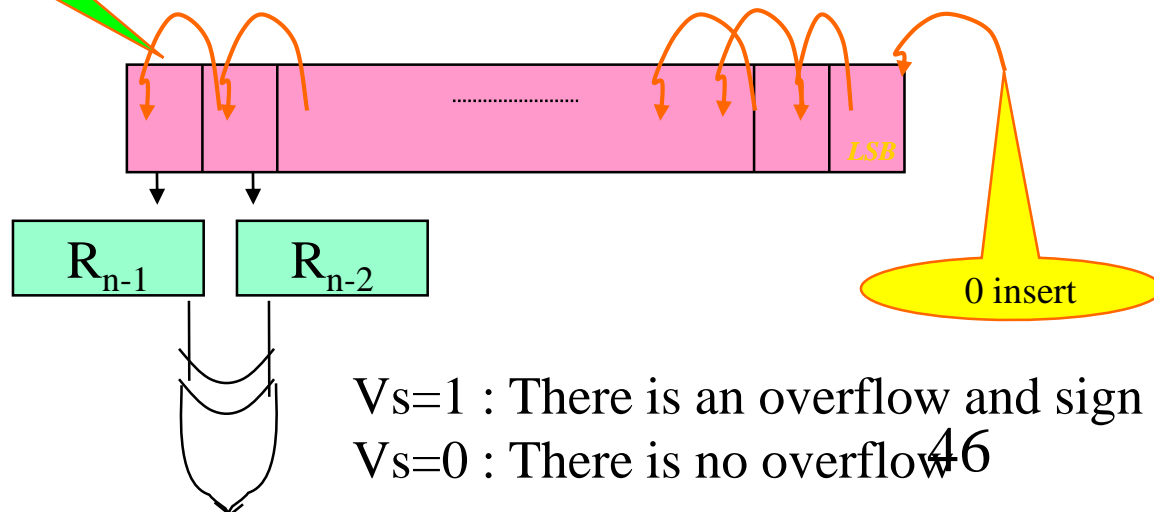

4-6 Shift Microoperations

Arithmetic Shifts

- Arithmetic Shift Left :

- Example 1

0010 (2) → 0100 (4)

- Example 2

1110 (-2) → 1100 (-4)

- Arithmetic Shift Left :

- Example 3

0100 (4) → 1000 (overflow)

- Example 4

1010 (-6) → 0100 (overflow)

4-6 Shift Microoperations ^{cont.}

- Example: Assume $R1 = 11001110$, then:
 - Arithmetic shift right once : $R1 = 11100111$
 - Arithmetic shift right twice : $R1 = 11110011$
 - Arithmetic shift left once : $R1 = 10011100$
 - Arithmetic shift left twice : $R1 = 00111000$
 - Logical shift right once : $R1 = 01100111$
 - Logical shift left once : $R1 = 10011100$
 - Circular shift right once : $R1 = 01100111$
 - Circular shift left once : $R1 = 10011101$